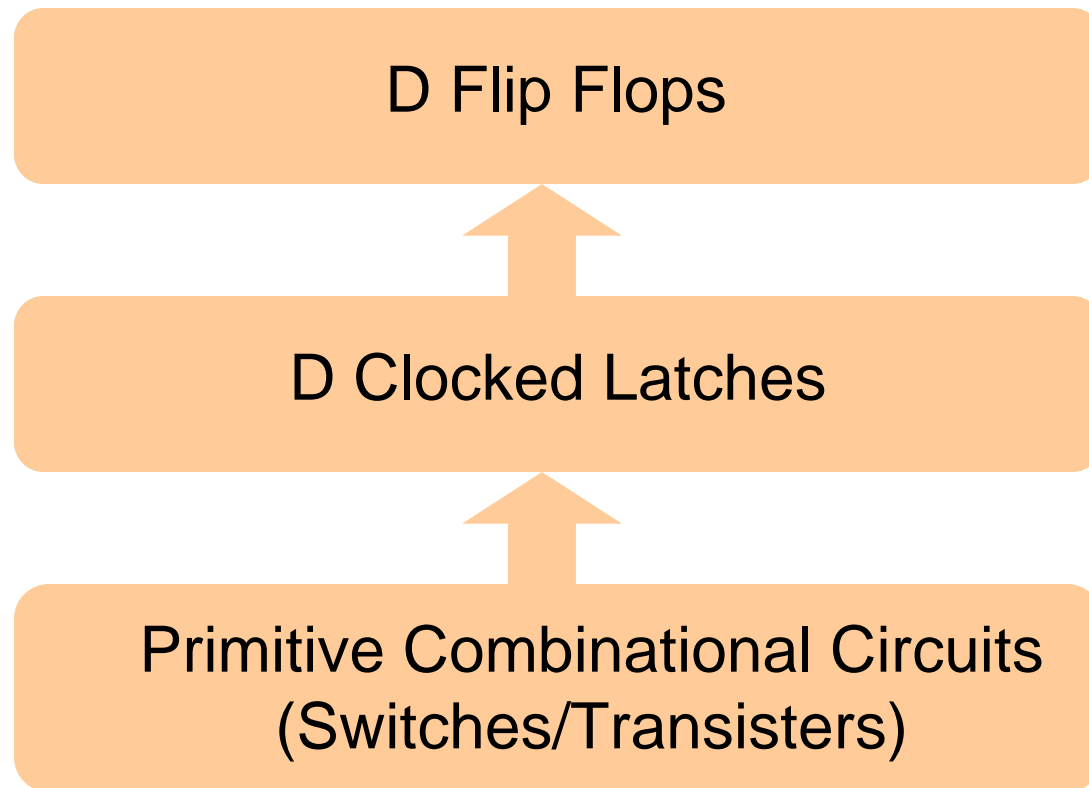


# Building D Flip Flops

- Combinational Circuit Components
  - Switches
  - Voltage inverters
- D Clocked Latch
  - Feedback to store bits
- D Flip Flop
  - Two D clocked latches




# Building D Flip Flops




# Combinational Circuit Components

Normally Open Switch

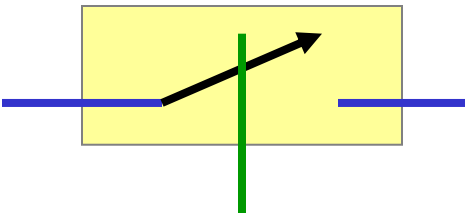


Normally Closed Switch

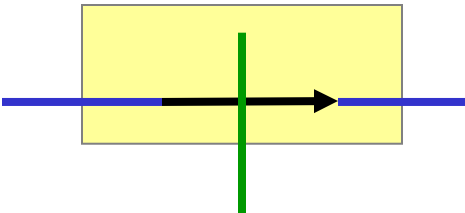


Galen Sasaki

Control = L

open

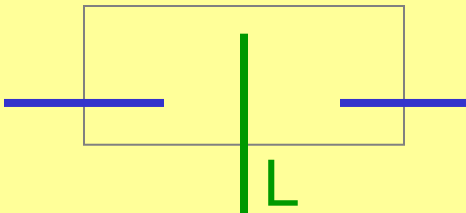


closed

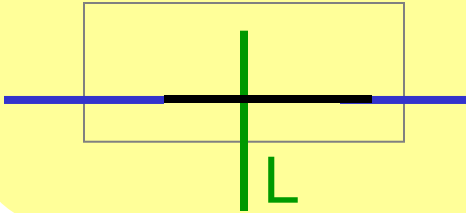


Control = H

closed

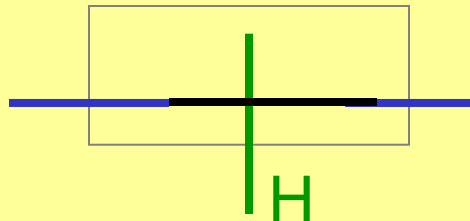

open

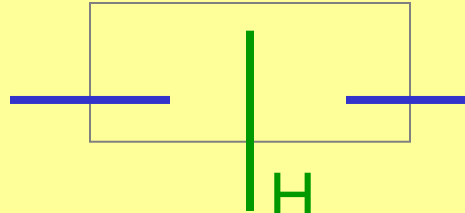



EE 260 University of Hawaii

3





# Combinational Circuit Components

Voltage Inverters  
(2 symbols)

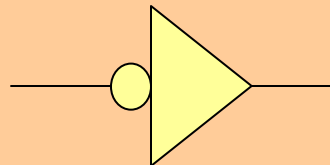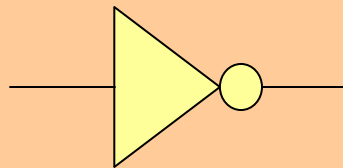


Active Device

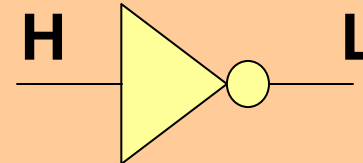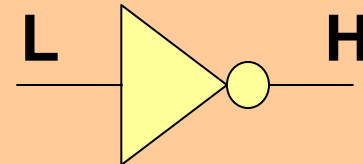

# A Simple 1-Bit Memory



# A Simple 1-Bit Memory

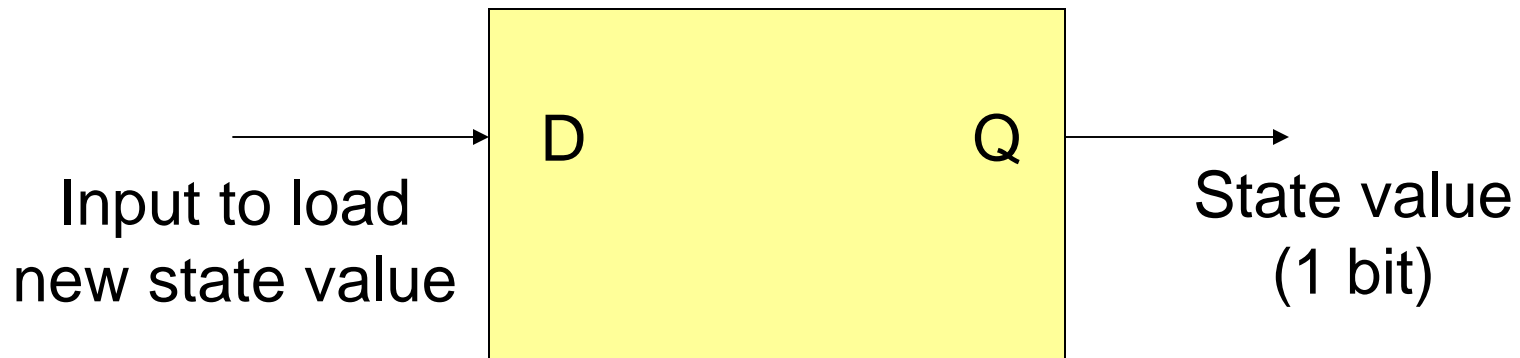

Two configurations:


Hold (store) = hold onto the state value

Load = load a new state value




# Holding (Storing) With Voltage Inverters

Devices drive each other

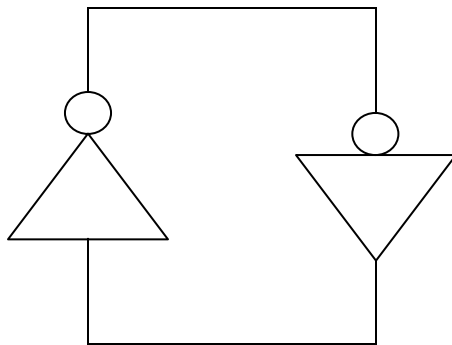

# Holding (Storing) With Voltage Inverters


Devices drive each other

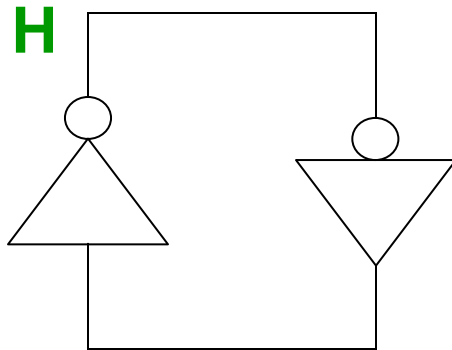




# Holding (Storing) With Voltage Inverters

Devices drive each other

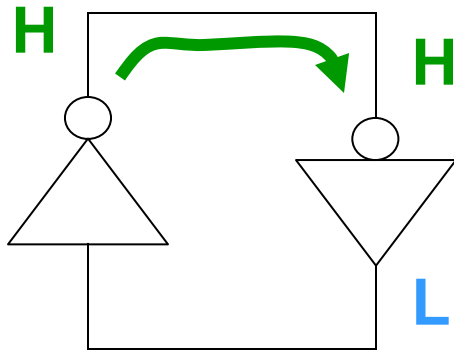



# Holding (Storing) With Voltage Inverters

Devices drive each other

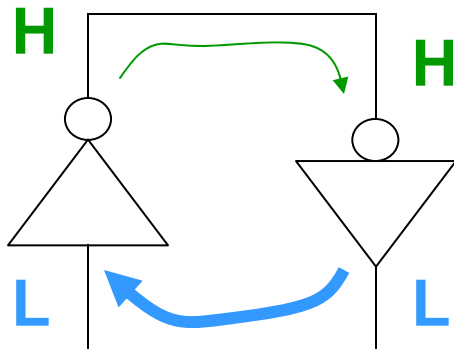

# Holding (Storing) With Voltage Inverters

Devices drive each other

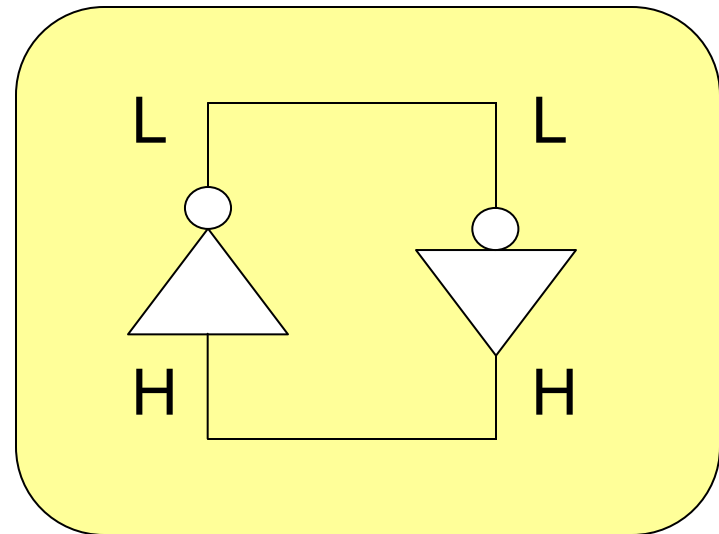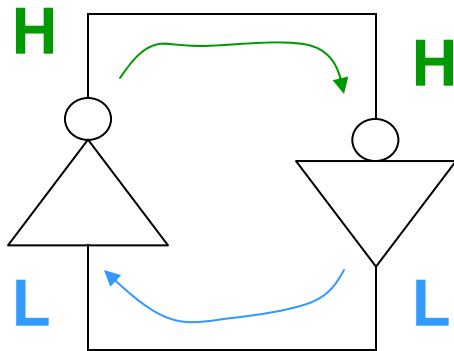

# Simple Memory: Two Configurations



Two configurations:


Hold (store) = hold onto the state value

Load = load a new state value




# Simple Memory: Two Configurations


Hold

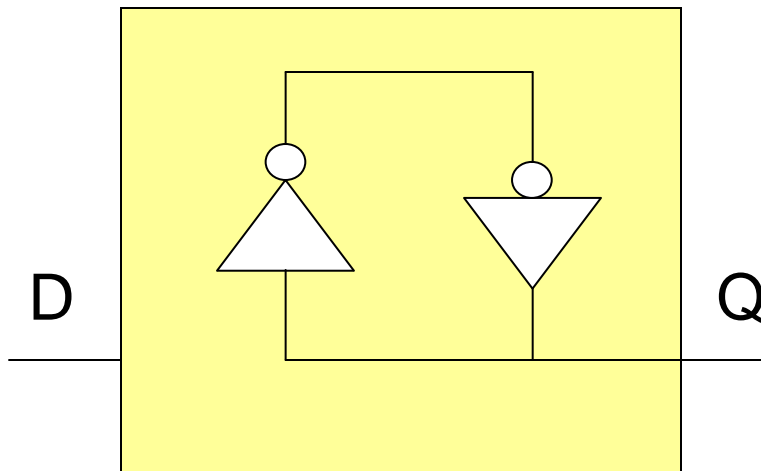


Load

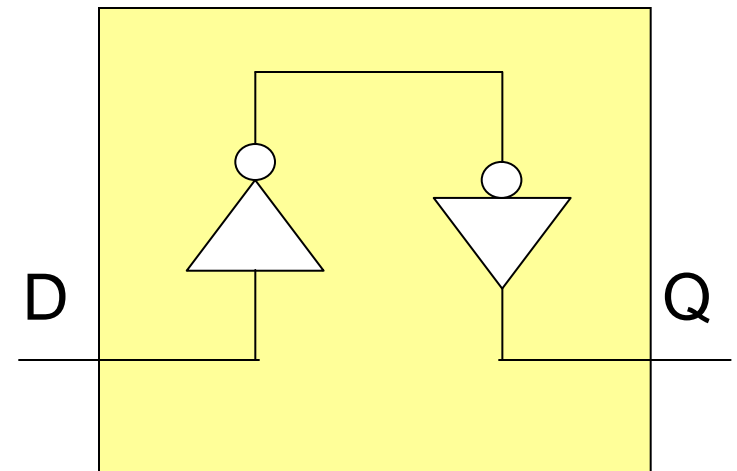

# Simple Memory: Two Configurations

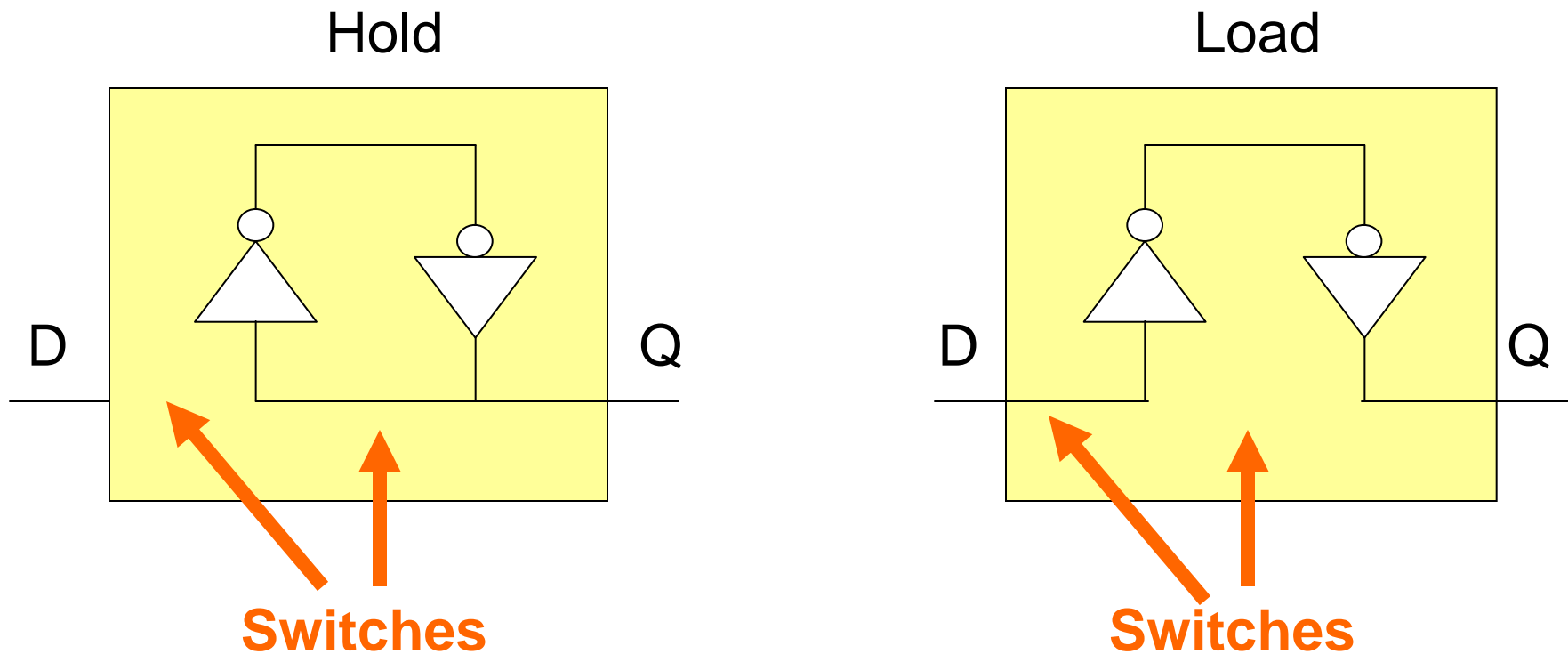

# D Clocked Latch

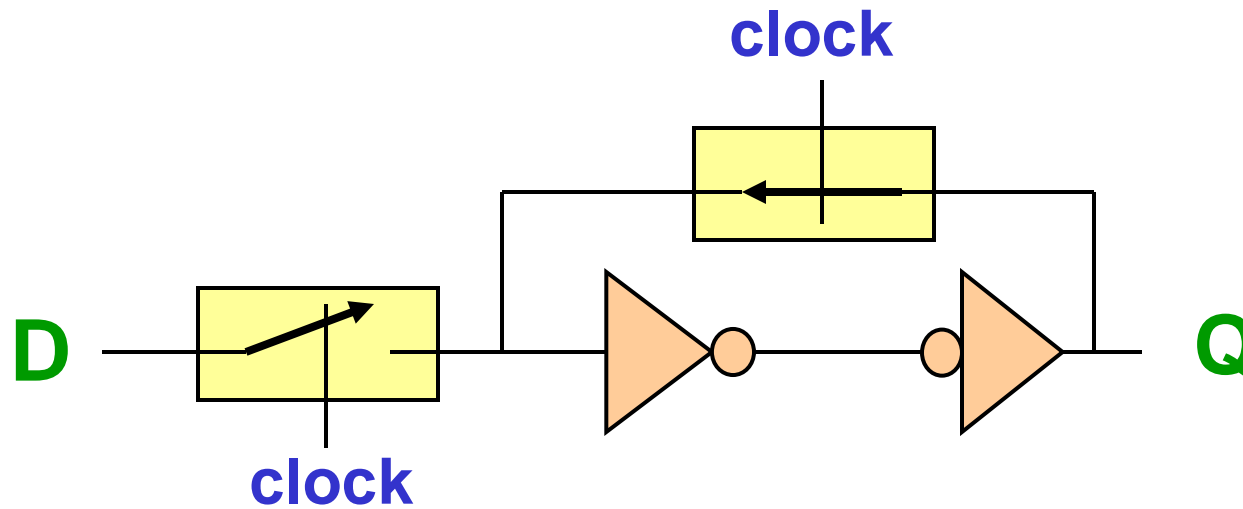


**clock = L : Hold**



**clock = H : Load**



# D Clocked Latch

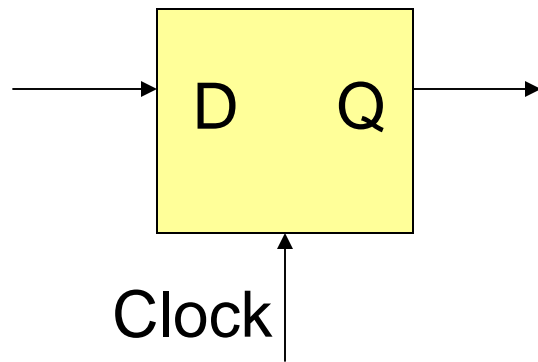

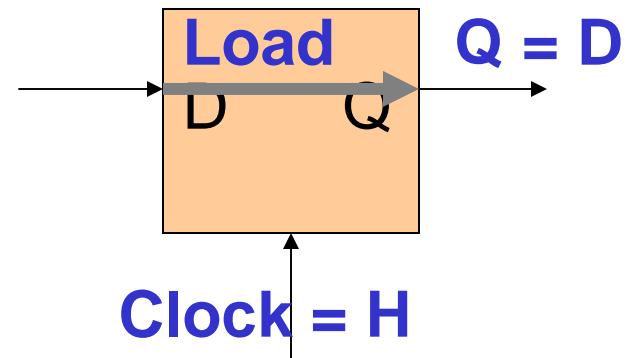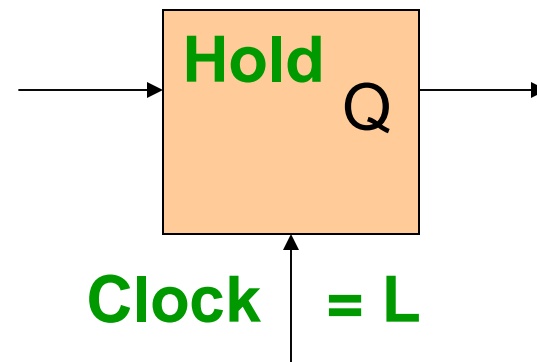It similar to a D flip flop  
but it reacts to the clock  
differently




It's "transparent"







# Comparing Flip Flop and Latch

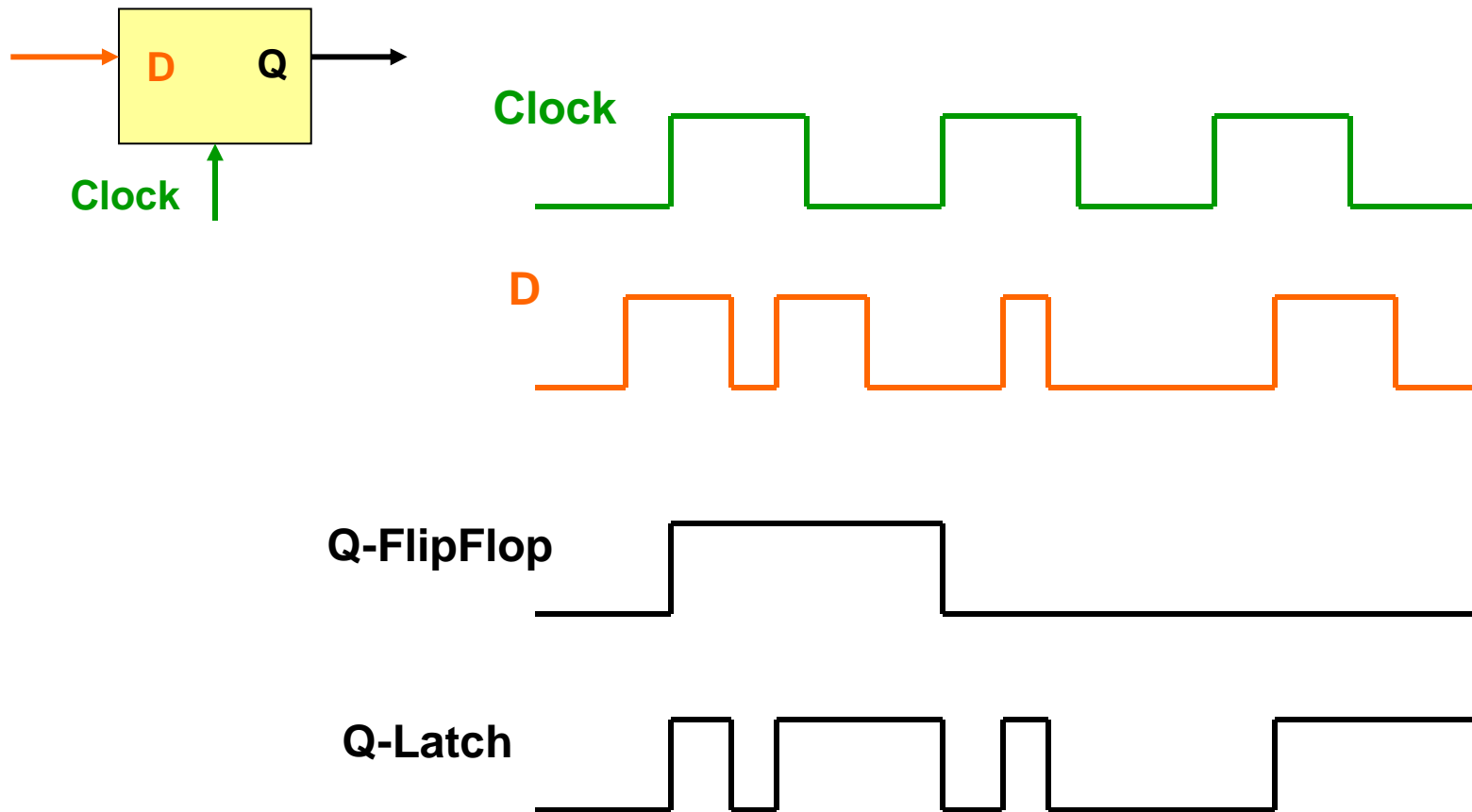


# Comparing Flip Flop and Latch

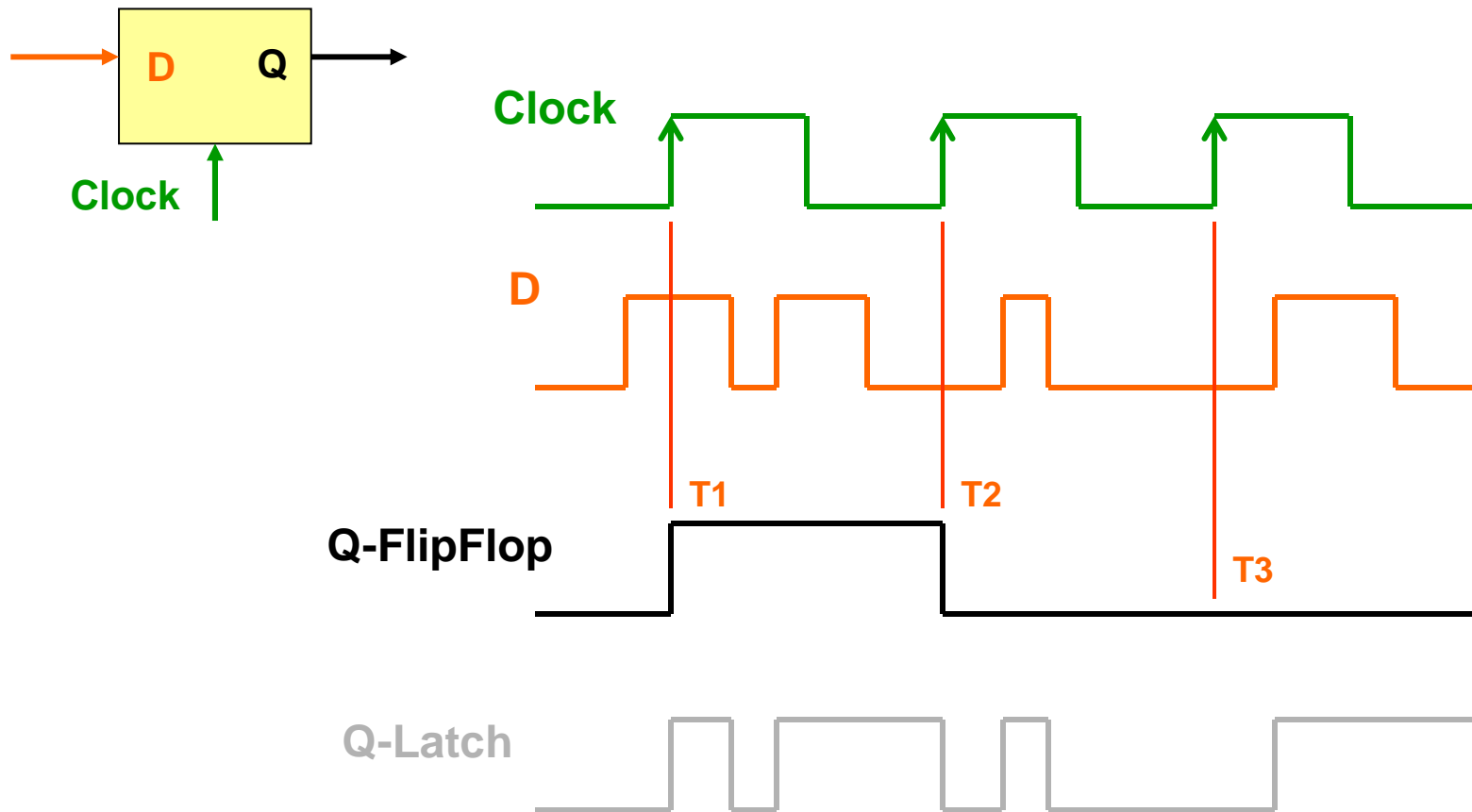

# Comparing Flip Flop and Latch

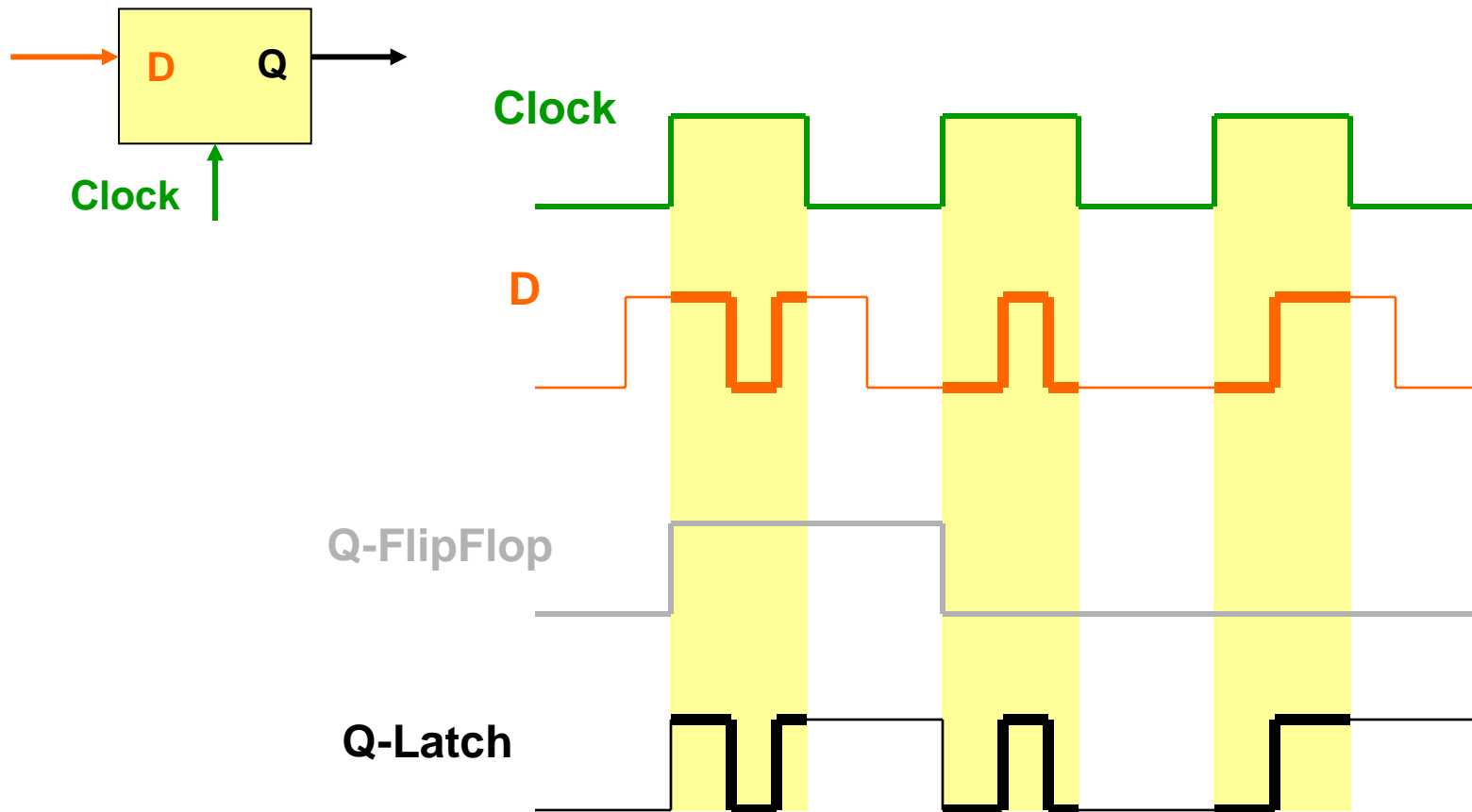

# Comparing Flip Flop and Latch

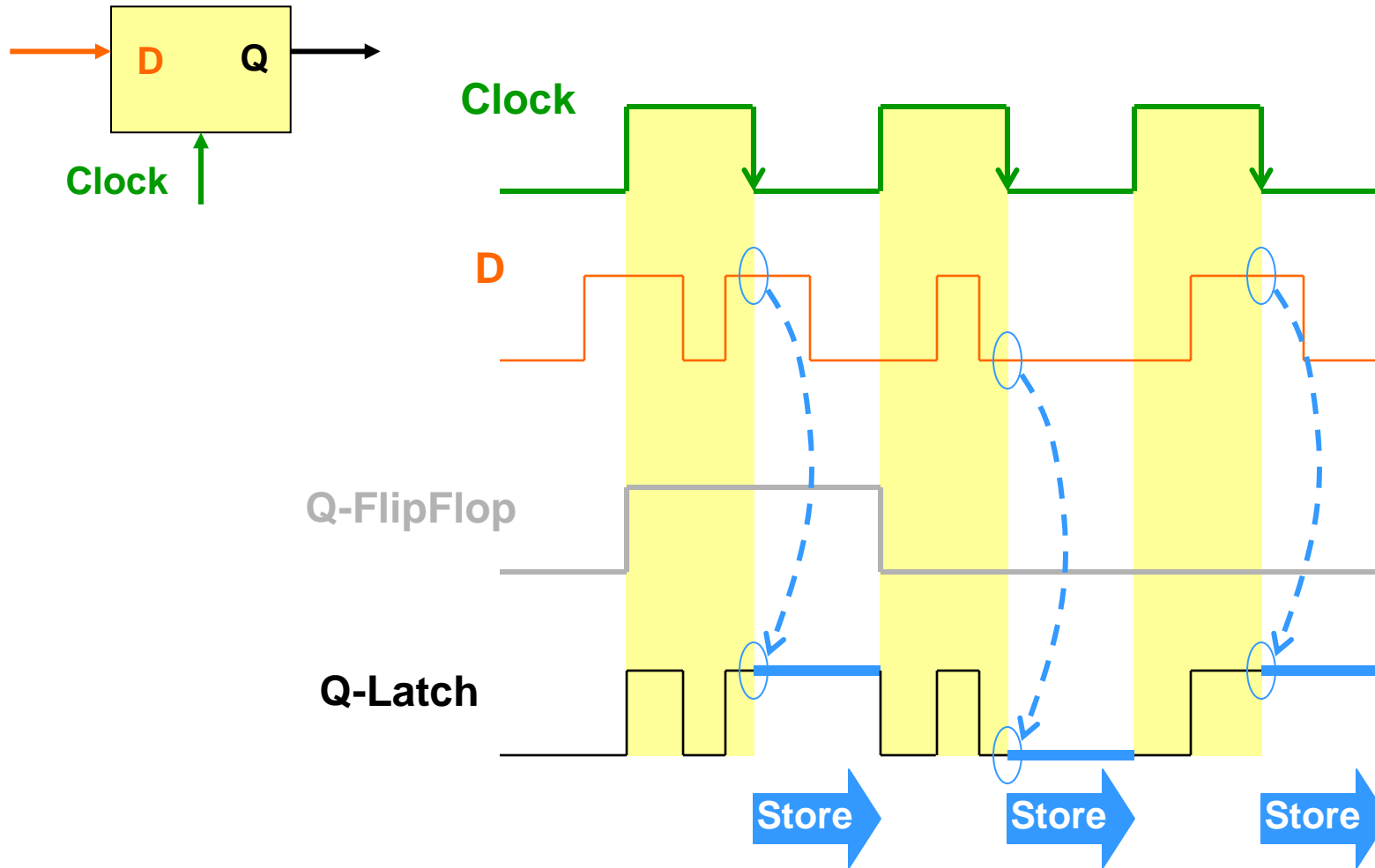


# D Flip Flop vs. D Clocked Latch


- D flip flop
  - Triggered on positive edge of clock
  - Output Q (and state) changes only at a *time instant*
- D clocked latch
  - Output Q changes (with D) while clock is H
  - Output Q changes during a *window of time*
  - Trickier to use since lots of changes can happen during a time duration
    - Flip flops are preferred to latches in designing circuits
    - Latches are used in memory circuits, e.g., RAM



# D Flip Flop

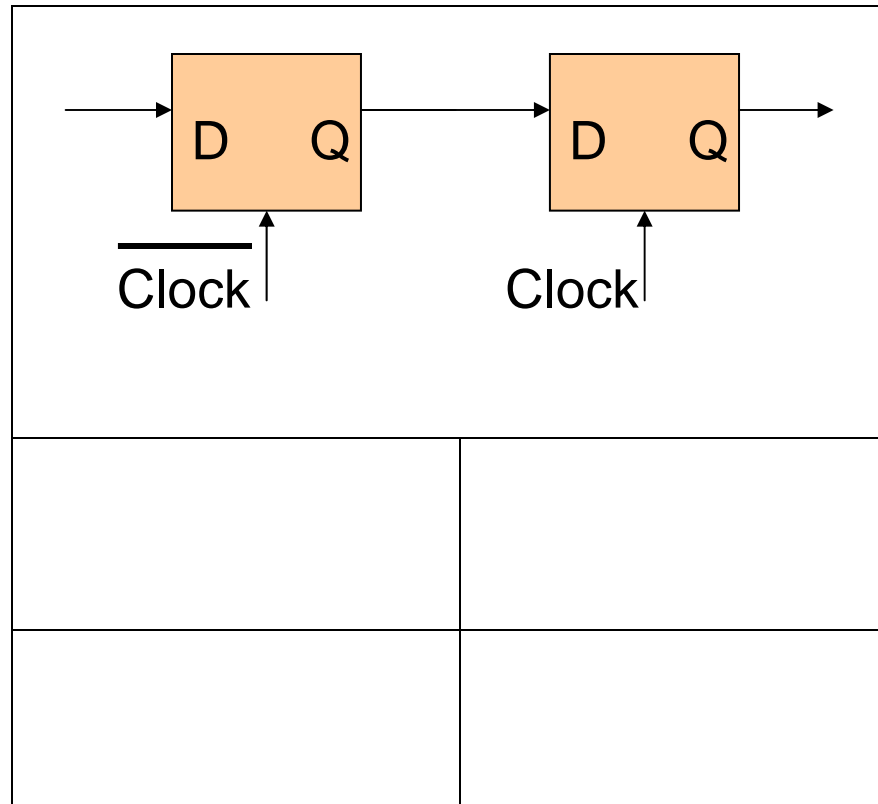


# D Flip Flop

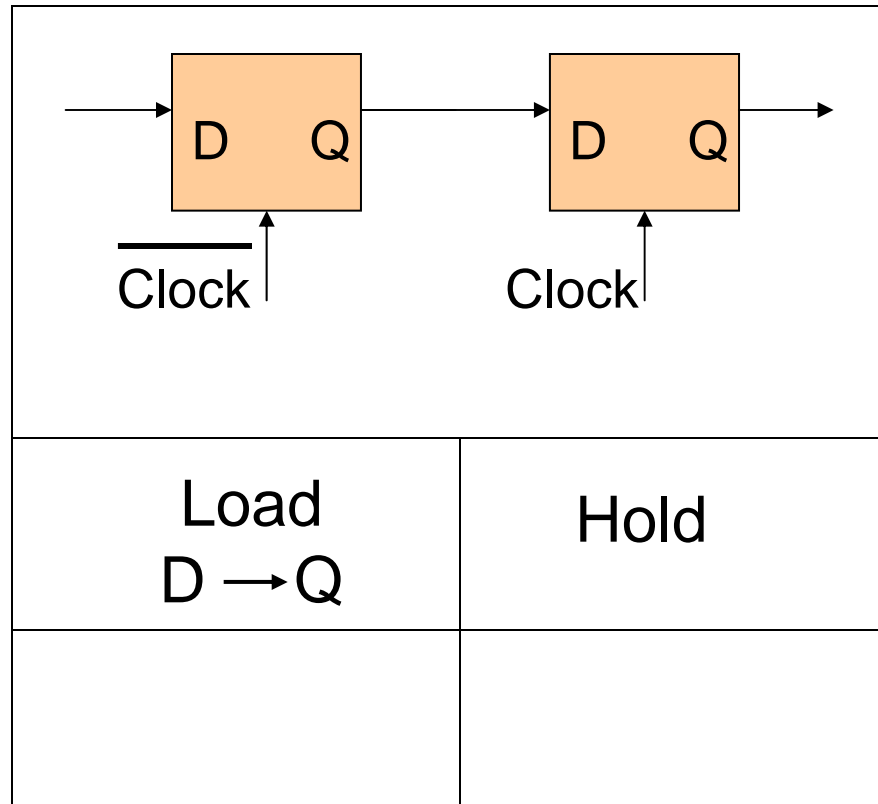

Clock = L




# D Flip Flop

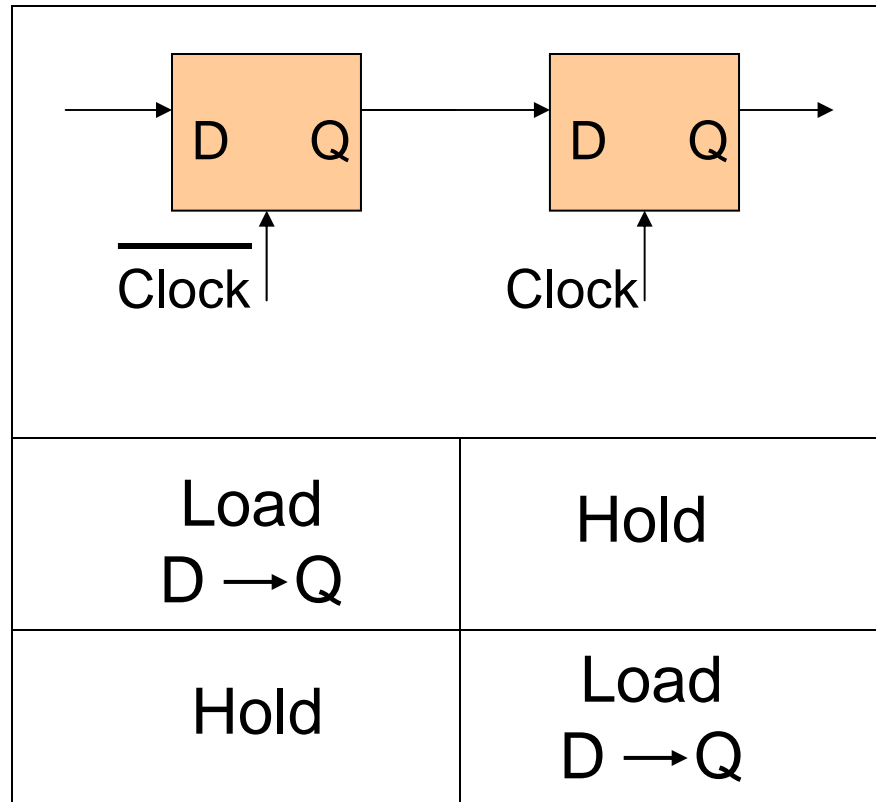





# D Flip Flop

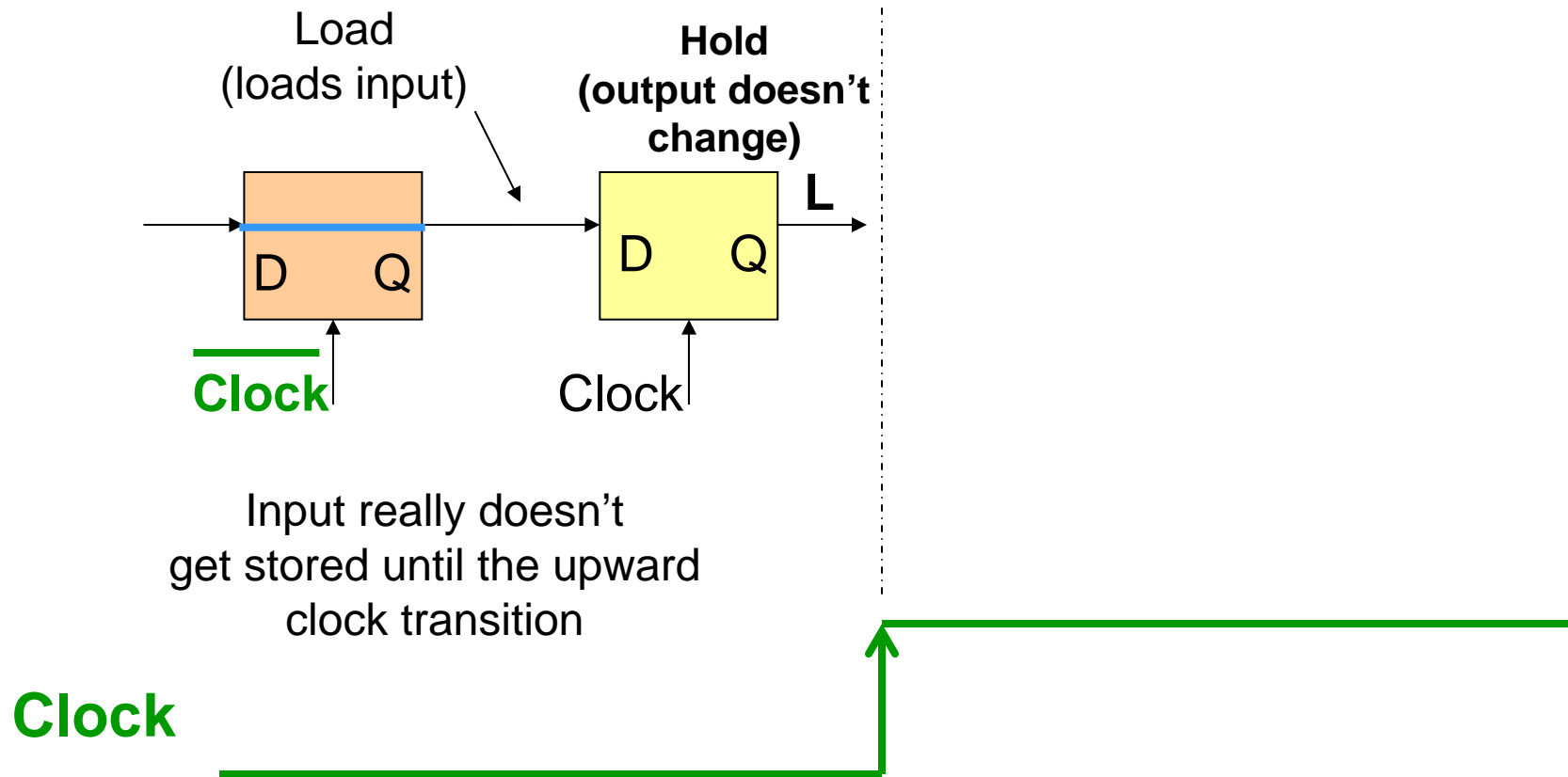

# D Flip Flop

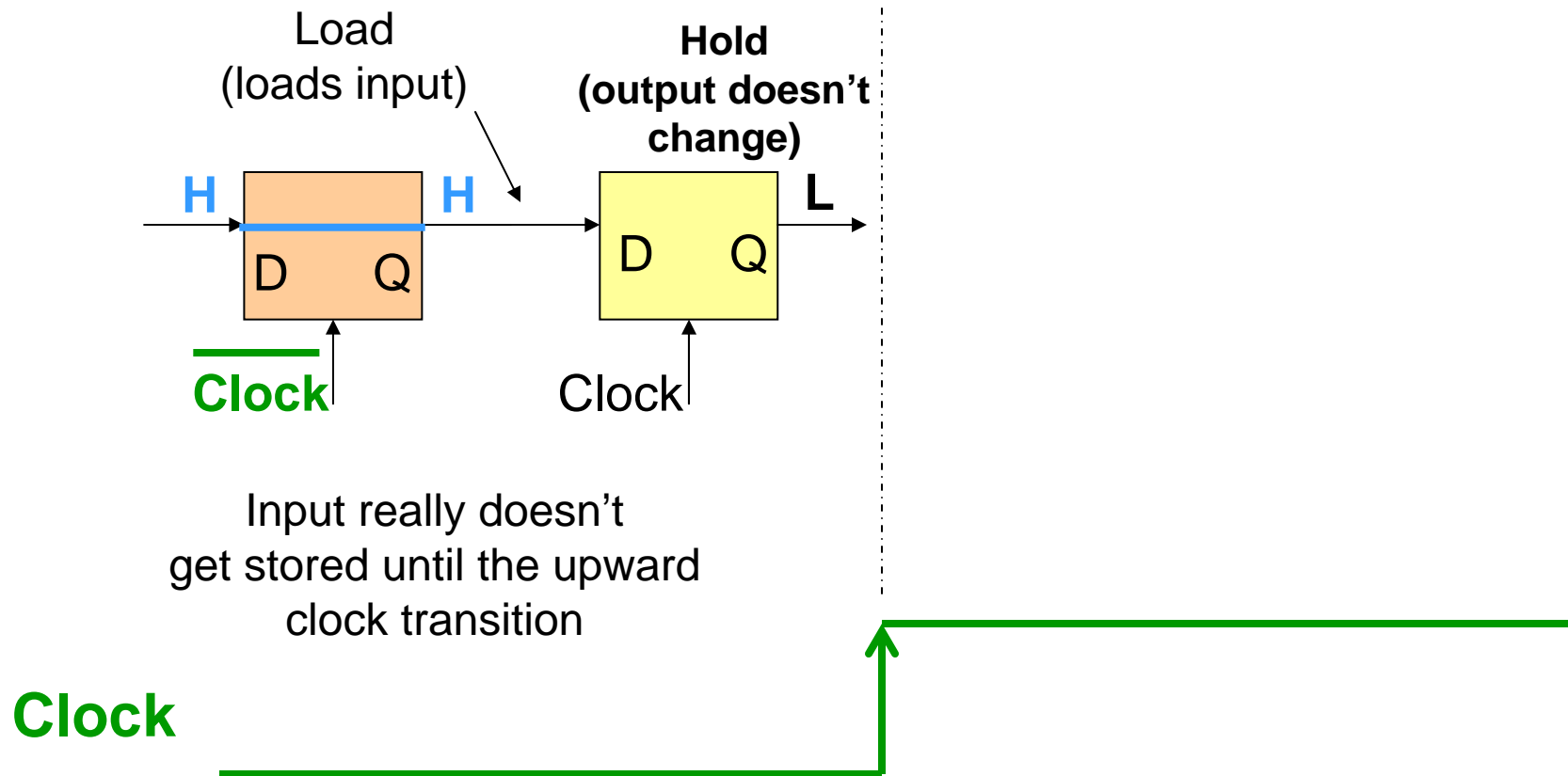

# D Flip Flop

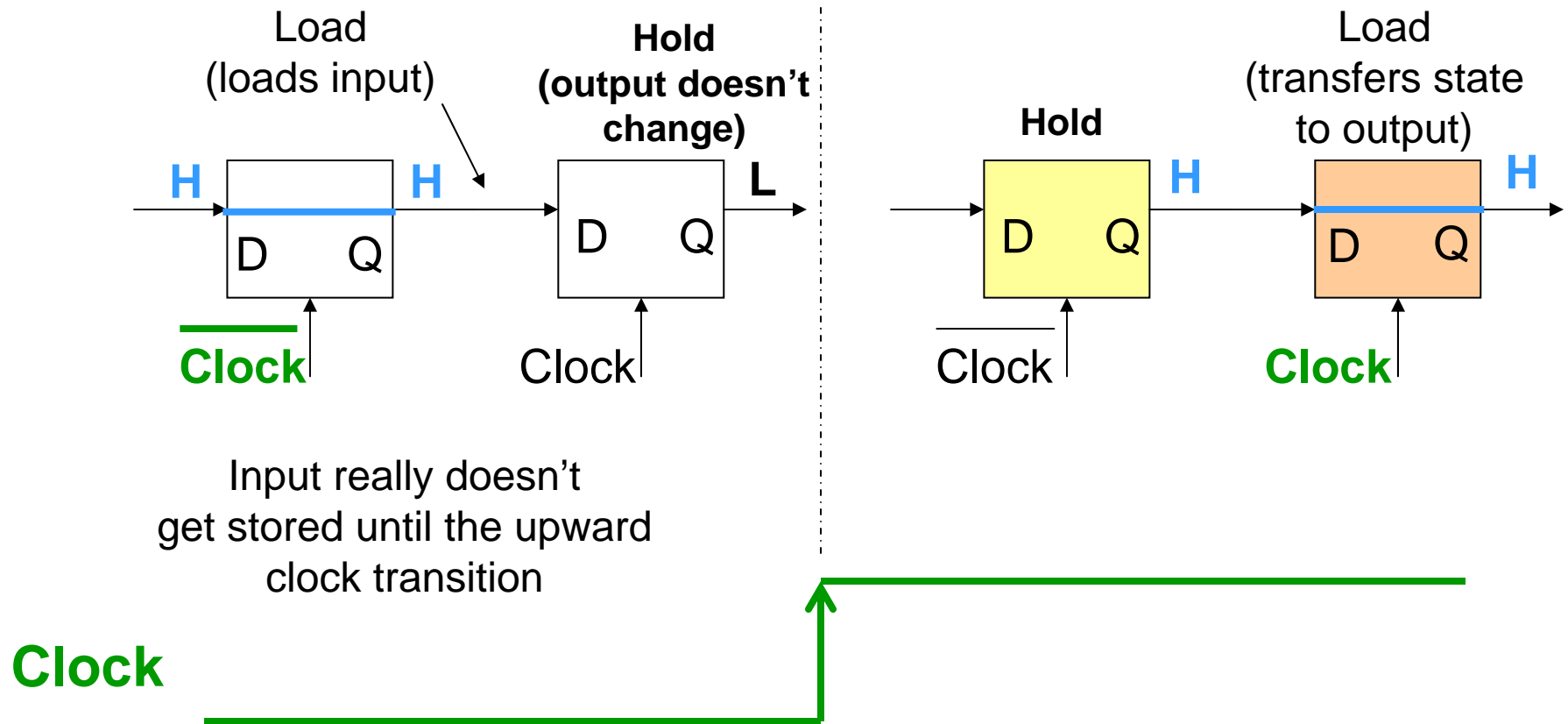

# Summary

- Combinational circuit components
  - switches and voltage inverters
- D clocked latch
  - Built from switches and voltage inverters
  - 2 configurations: load and hold
- D flip flop
  - Built from two D latches in series

